

Buck Converter SS Analysis

Given Requirements

V_{in}	D_{on}	f_{sw}	L	R	C
12 V	42%	10^5 Hz	10^{-4} H	10Ω	3.3×10^{-6} f

$$AVG(v_o) = V_{in} D_{on} = 5.04 \text{ V}$$

$$\Delta I_L = \frac{v_o}{L} T_{down}$$

$$T_{down} = \frac{1}{f_{sw}} (1 - D_{on})$$

$$\Delta I_L = \frac{v_o}{L f_{sw}} (1 - D_{on}) = \frac{5.04}{10} \times 0.58 = 292 \text{ mA}$$

$$AVG(i_L) = \frac{v_o}{R} = 504 \text{ mA}$$



Condition of CCM $AVG(i_L) \geq \frac{\Delta I_L}{2}$ as this condition has been met the converter is running in CCM Mode.

Boundary of CCM and DCM occurs at $AVG(i_L) = \frac{\Delta I_L}{2}$

$$R_c = \frac{2v_o}{\Delta I_L} = 34.5 \Omega$$

$$\Delta V_o = \frac{\Delta I_L}{8C f_{sw}} = 111 \text{ mV}$$

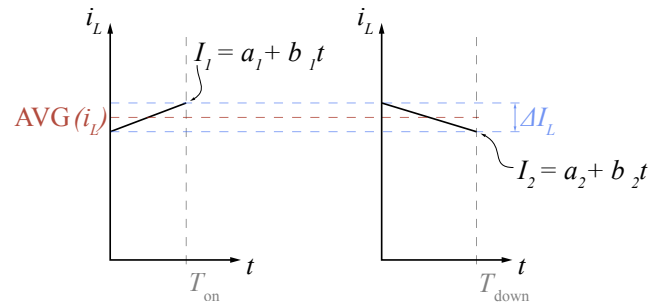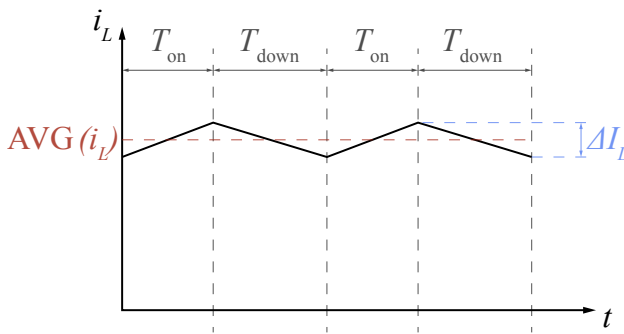Consider the current in the inductor (I_L) over time.



$$I_n = a_n + b_n t$$

$$RMS(i_L) = \sqrt{f_{sw} (\int_0^{T_{on}} I_1^2 dt + \int_0^{T_{down}} I_2^2 dt)}$$

$$r_n(T) = \int_0^T I_n^2 dt = \frac{1}{3} b_n^2 T^3 + a_n b_n T^2 + a_n^2 T$$

$$a_1 = AVG(i_L) - \frac{1}{2} \Delta I_L$$

$$a_2 = AVG(i_L) + \frac{1}{2} \Delta I_L$$

$$b_1 = \frac{\Delta I_L}{T_{on}}$$

$$b_2 = -\frac{\Delta I_L}{T_{down}}$$

$$RMS(i_L) = \sqrt{f_{sw} (r_1(T_{on}) + r_2(T_{down}))} = 337 \text{ mA}$$

Buck Converter Simulation

From the circuit diagram we can see

$$i_L = i_{co} + \frac{v_o}{R}.$$

It can be found that

$$i_L = \frac{1}{L} \int (V_{in} - v_o) dt \text{ in the on state,}$$

$$i_L = \frac{1}{L} \int -v_o dt \text{ in the down state and}$$

$$i_{co} = C \frac{dv_o}{dt} \text{ in both states.}$$

Consider a square wave signal

$$p(t) = \begin{cases} 0 & \text{on state} \\ 1 & \text{off state} \end{cases}$$

that meets the desired PWM requirements.



$$i_L = \frac{1}{L} \int (V_{in}p - v_o) dt$$

$$\frac{1}{L} \int (V_{in}p - v_o) dt = C \frac{dv_o}{dt} + \frac{v_o}{R}$$


Integrating the equation and rearranging gives

$$v_o = \frac{1}{C_o} \left(\frac{1}{L} \left(\iint (V_{in}p - v_o) - \frac{1}{R} \int v_o \right) \right) \text{ with integrals in terms of } dt.$$

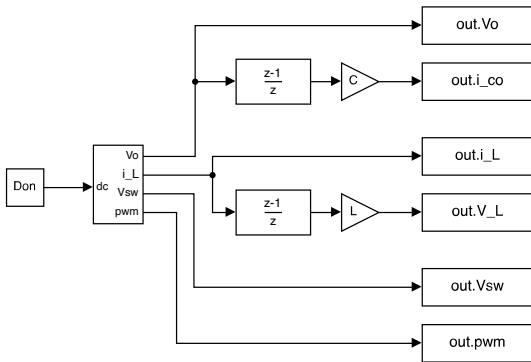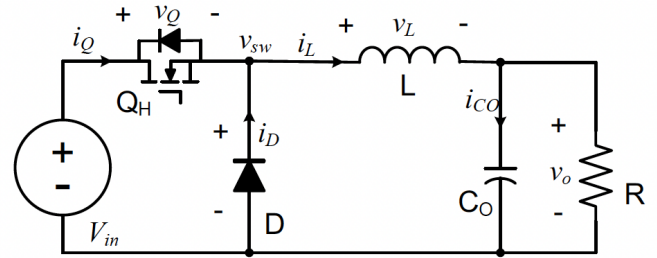From which the following simulation and subsystem was made in MATLAB's simulink.











Buck converter simulation block.

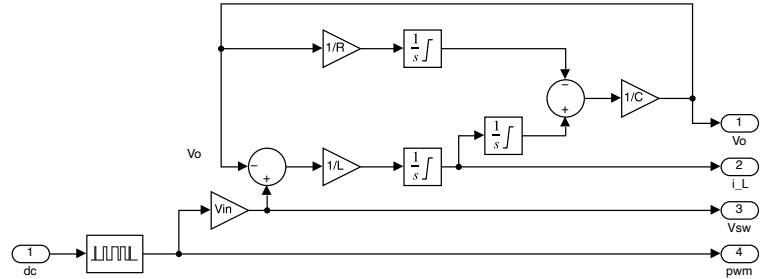

Buck converter simulation subsystem.

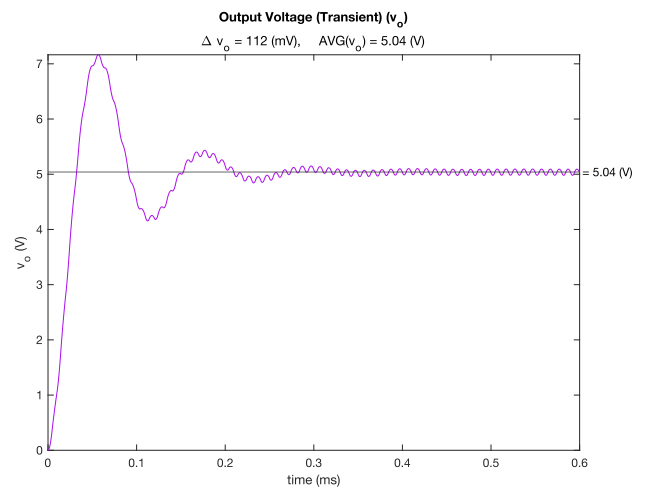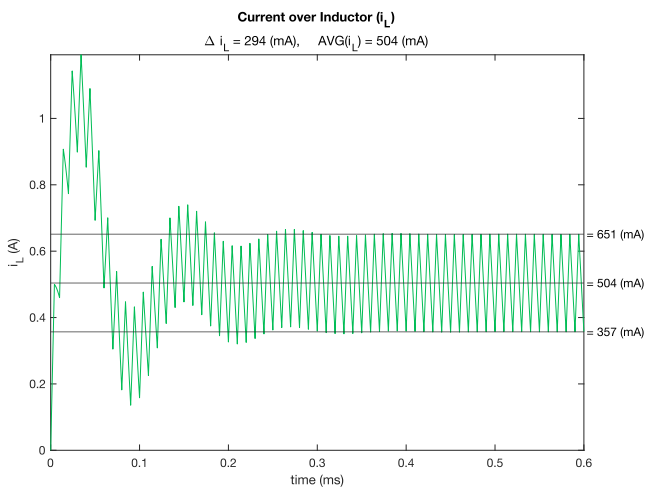Simulation duration was set to 1 ms (though only 0.6 ms was shown in graphs) and the simulation step duration was set to $\frac{1}{1000f_{sw}}$ s.



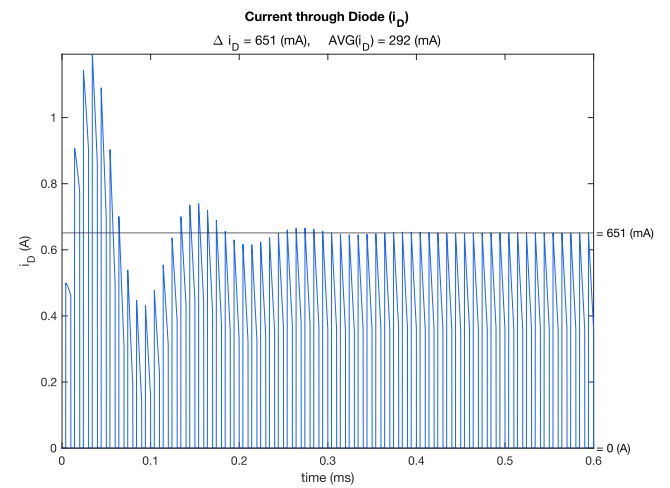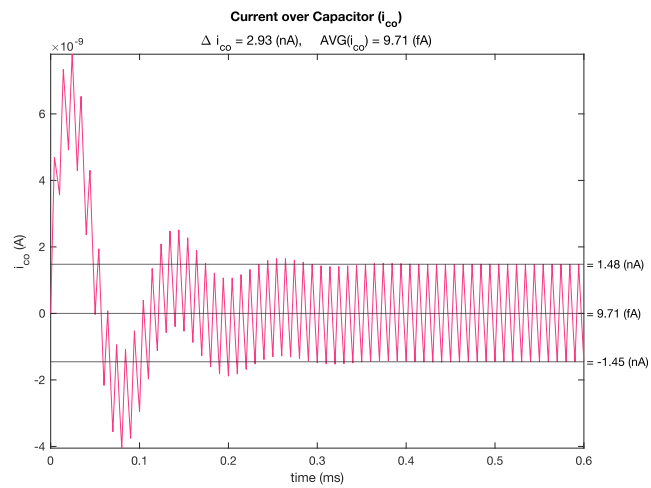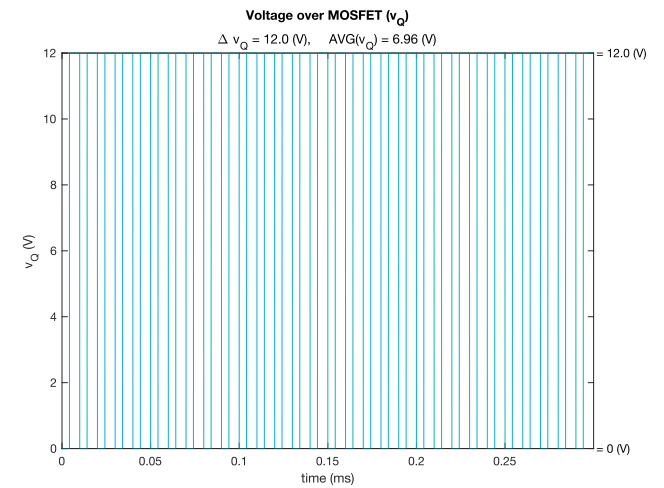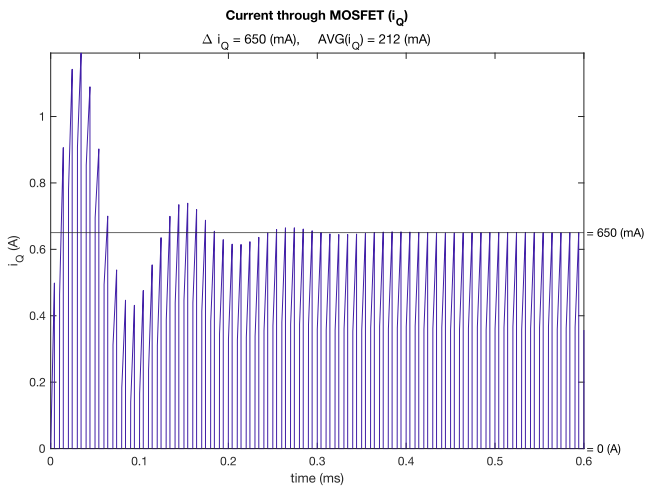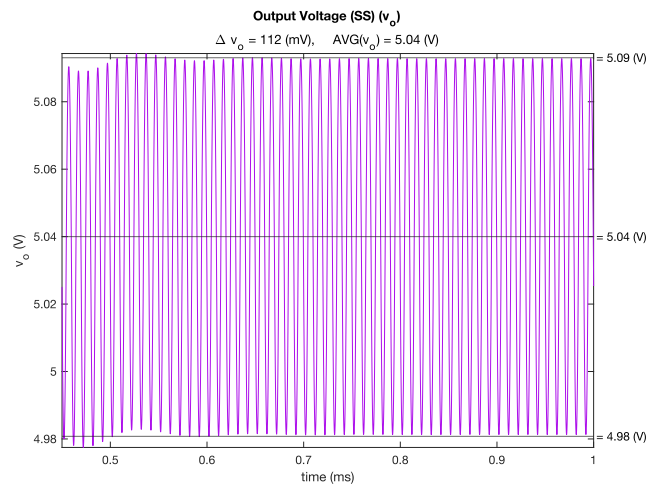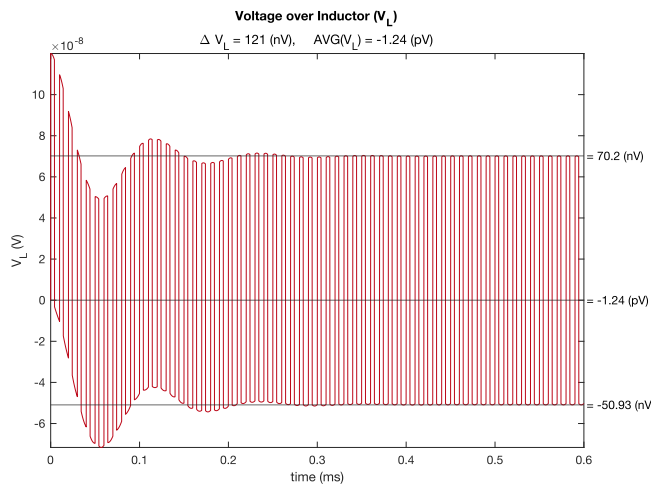

As can be seen, the results of the simulation accurately (to roughly 3 S.F.) match those calculated from the steady state analysis.

MATLAB Code Appendix

```
clc;
Vin = 12;
Don = 0.42;
fsw = 10^5;
L = 1e-4;
R = 10;
C = 3.3e-6;

AVG_v_o = Vin * Don;
fprintf("AVG(v_o) = %s\n", funit(AVG_v_o, "V"));

Tdown = (1/fsw) * (1 - Don);
Ton = (1/fsw) * Don;
DI_L = Tdown * AVG_v_o / L;
fprintf("ΔI_L = %s\n", funit(DI_L, "A"));

AVG_I_L = AVG_v_o / R;
fprintf("AVG(I_L) = %s\n", funit(AVG_I_L, "A"));

a1 = DI_L - 0.5 * AVG_I_L;
a2 = DI_L + 0.5 * AVG_I_L;
b1 = DI_L/Ton;
b2 = -DI_L/Tdown;
rmss1 = Ton * a1^2 + (1/3) * b1^2 * Ton^3 + a1 * b1 * Ton^2;
rmss2 = Tdown * a2^2 + (1/3) * b2^2 * Tdown^3 + a2 * b2 * Tdown^2;
rms = sqrt(fsw * (rmss1 + rmss2));
fprintf("RMS = %s\n", funit(rms, "A"))

Rc = 2 * AVG_v_o / (DI_L);
fprintf("R_c = %s\n", funit(Rc, "Ohms"));

DVo = DI_L/(8 * C * fsw);
fprintf("DV_o = %s\n", funit(DVo, "V"));

time = out.V_L.time * 1000; %ms

V_L = out.V_L.signals.values;
Vo = out.Vo.signals.values;
Vsw = out.Vsw.signals.values;
i_L = out.i_L.signals.values; % mA
i_co = out.i_co.signals.values;
pwm = out.pwm.signals.values;
i_D = i_L .* (1 - pwm);
i_Q = i_L .* pwm;
V_Q = (1 - pwm) .* Vin;
```

```
%% Plot Simulation Signals
```

```
colors = [  
    2, 189, 86;  
    173, 16, 235;  
    250, 55, 130;  
    189, 8, 25;  
    163, 139, 16;  
    0, 182, 207;  
    28, 99, 252;  
    66, 32, 168;  
]/255;
```

```
% MAKE PLOT  
color = colors(8,:);  
showbounds = 1;  
showavg = 0;  
sigunit = "A";  
signame = "i_{Q}";  
ptitle = "Current through MOSFET";  
sig = i_Q;  
trans_range = round(length(time) * 0.6):length(time);  
range = 1:round(length(time) * 0.6);  
% range = round(length(time) * 0.45):round(length(time) * 1);
```

```
tinc = (time(range(end)) - time(range(1)))/100;
```

```
avg = mean(sig(trans_range));  
maxi = max(sig(trans_range));  
mini = min(sig(trans_range));
```

```
plot(time(range), sig(range), "Color", color);  
xlabel("time (ms)");  
ylabel(sprintf("%s (%s)", signame, sigunit));  
axis([min(time(range)), max(time(range)), min(sig(range)), max(sig(range))]);  
title(sprintf("%s (%s)", ptitle, signame));  
subtitle(sprintf("\Delta %s = %s, AVG(%s) = %s", signame, funit(maxi - mini, sigunit), signame,  
funit(avg, sigunit)));
```

```
if (showavg)  
    yline(avg);  
    text(time(range(end)) + .5*tinc, avg, sprintf("= %s", funit(avg, sigunit)));  
end
```

```
if (showbounds)  
    yline(maxi);  
    yline(mini);  
  
    text(time(range(end)) + .5*tinc, maxi, sprintf("= %s", funit(maxi, sigunit)));  
    text(time(range(end)) + .5*tinc, mini, sprintf("= %s", funit(mini, sigunit)));
```

end

```
pos = get(gca, 'Position');
pos(1) = 0.1;
pos(3) = 0.80;
set(gca, 'Position', pos);
```

```
%% Create Sim Figures
handle=get_param('bucksim/Subsystem','handle');
print(handle,'-dsvg','fig-sim-sub');
```

```
handle=get_param('bucksim','handle');
print(handle,'-dsvg','fig-sim');
%%
```

```
function str = funit(value, qty)
    num = value;
    unum = 0;
    if num == 0
        str = sprintf("0 (%s)", qty);
    else
        while (num > 1000)
            num = num / 1000;
            unum = unum + 1;
        end
        while (abs(num) < 1)
            num = num * 1000;
            unum = unum - 1;
        end

        unitsa = ['k', 'M', 'G', 'T'];
        unitsb = ['m', 'u', 'n', 'p', 'f'];
        if (unum < 0)
            unum = unitsb(-unum);
        elseif (unum > 0)
            unum = unitsa(unum);
        else
            unum = "";
        end

        dp = 0;
        if (num < 10); dp = 2;
        elseif (num < 100); dp = 1;
        end
        str = sprintf(sprintf("%%%.%df (%%c%%s)", dp), num, unum, qty);
    end
end
```