

1 Converter Circuit Description and Specifications

The schematic of the buck converter is shown Figure 1. The PCB board has been fabricated to be used directly. The connection is described as:

- The pin-4 and Pin-5 of the terminal box J3 on the board shall connected to the PWM signals from the microcontroller that you are using.
- These PWM signals are then boosted by the MOSFET driver UCC27211 to control the gates of two MOSFETs Q1 and Q2.
- An inductor needs to be connected the terminals J1 and J2.
- The positive terminal for the DC source is P1. It is from a programmable DC power supply.
- The common ground for both the source and load is connected to P3. The testing point of ground is TP7 for the probe connection.
- The positive terminal for the load connection is P2. We use a resistive load.

The circuit specification of the buck converter is the same as the first assignment.

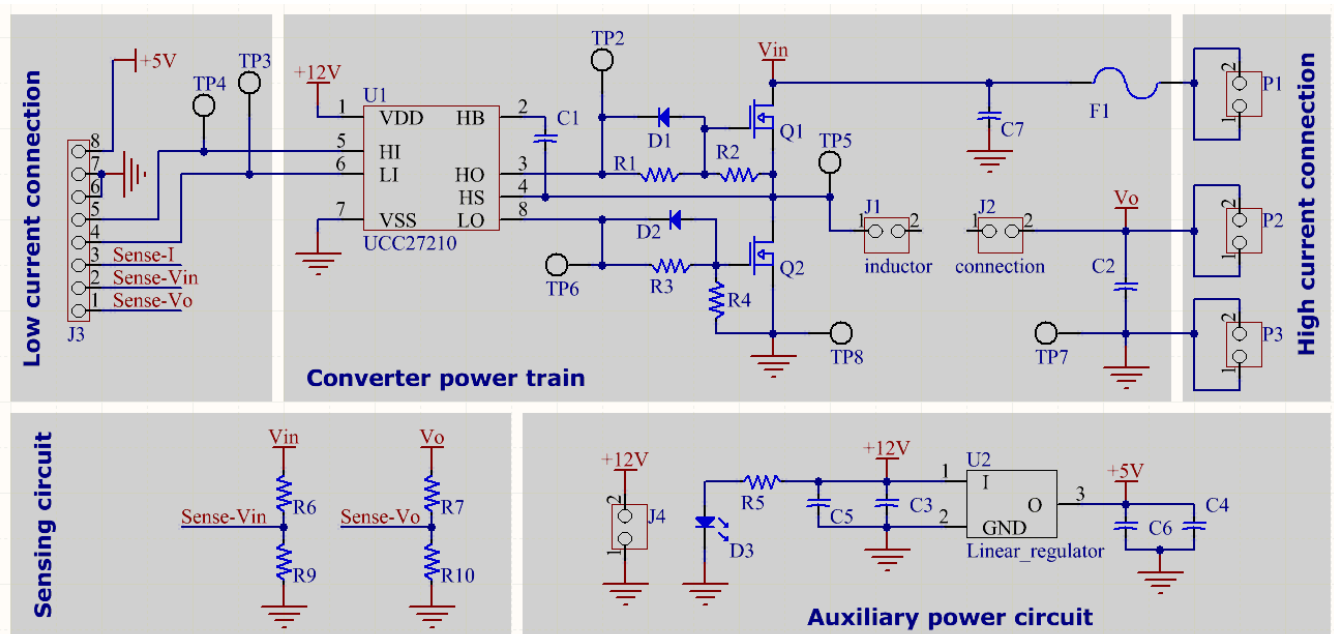


Figure 1 Circuit schematics

2 Construct DC/DC converter

- 1) According to the magnetic core datasheet make winding to construct one inductor to meet the inductance requirement, which is determined by the concept design.
- 2) Use LCR meter to check and confirm the inductance value and its ESR value.
- 3) According to the converter schematics, as shown in Figure 1, identify the board connection of V_{in+} , V_{in-} , V_{o+} , and V_{o-} .
- 4) According to the converter schematics, as shown in Figure 1, identify the board connection of the auxiliary power supply for the 12V DC.
- 5) According to the converter schematics, as shown in Figure 1, identify the board connection of the interlinking inductor.
- 6) According to the converter schematics, as shown in Figure 1, identify the location and meaning of the test point.
- 7) According to the converter schematics, as shown in Figure 1, identify the location and meaning of the control signals.
- 8) Connect to the load with the rated resistance.
- 9) The driver IC can be either UCC27210 or UCC27211. They are the same for your application.
- 10) Consult with tutor for any support.

3 Power Up Procedure

3.1 Precheck

- Using the multimeter to check the input impedance and the output impedance of the converter to avoid short circuit.
- You should use it to check all connections according to the schematics before jumping into the next step.
- A common mistake is the grounding network. All ground should be connected together.

3.2 Power up gate driver circuit

- Connect J4 to the bench-top DC power supply. Be careful of the polarity marked on board.
- Gradually increase the voltage from 0 to 12V by the auxiliary power supply, which supply the FET driver.

3.3 Power up the microcontroller circuit

- Connect the converter board to the microcontroller board for the 5V, GND, and PWM signals.
- Program the microcontroller to generate the PWM signal with the specified duty cycle output.
- Review the converter schematics and the PCB board to find the assigned 4 test points on board for PWM signal detection.
- Use oscilloscope to check the PWM signals that are transmitted to the gate of both MOSFET.

3.4 Power up input voltage of converter

- The converter input port is P1 for positive and P3 for negative connection. Before powering up, consult with tutor after the connection.
- Use the Tektronix current probe and oscilloscope to monitor the inductor current, i_L and
- Connect a voltage probe to monitor the output voltage, v_o .
- Gradually increase the voltage of the DC power supply from 0 to the rated level V_{in} and observe the change of the waveforms of voltage and current. Keep the input voltage constant at the rated input voltage level, V_{in} .

4 Check and Test

4.1 At the rated power level

- Use USB flash drive to record the waveform image and dataset of the inductor current and output voltage. Ripple level of current and voltage should be clearly measured and recorded.
- Use USB flash drive to record the waveform image and dataset of the inductor current and switching node voltage, v_{sw} .
- Evaluate the conversion efficiency, P_{OUT}/P_{IN} , based on the rated load resistor.

4.2 At reduced power level

- Change the load resistor to 20 ohm. It can be done by series connecting two 10-ohm resistors. Make sure the connection is solid, not loose!

- Repeat the same for the waveforms and efficiency evaluation.
- Attention: stop the power supply of V_{in} for any change in circuit.

4.3 *At increased power level*

- Change the load resistor to 5 ohm. It can be done by paralleling two 10-ohm resistors.
- Repeat the same for the waveforms and efficiency evaluation.
- Attention: stop the power supply of V_{in} for any change in circuit.

5 **Demonstration and Finish**

- Demonstrate the testing process to one of the tutors.
- The tutor should prove your achievement of all required testing and evaluation.
- Disassemble the circuit and return the DC/DC converter board to tutor.

6 **Final Report**

The report should include the recorded information, comparisons of measurements, comments, and conclusions. The following is essential in the report.

- A description of the objective, experimental setup, and your expectation.
- A picture of the prototype board and the experimental setup.
- Clearly illustrate the recorded waveforms, the pulsating signals, i_L , and v_o .
- Compare the experimental results with the theoretical analysis and simulation results. Comment on the difference and agreement among them.
- Use a table to show the efficiency values of the three load conditions.
- Evaluate and check if the recorded waveforms meet your expectation and defend your judgment in the conclusion.